

The Metric Bridge

*Laws of the Metric Bridge Experiment:

* Calculating the Unknown Resistance R_x :

$$R_x = R \times L_1/L_2$$

R_x → is the unknown resistance.

R → is the known standard resistance.

L_1 → is the length of the wire from the starting point to the balance point.

L_2 → is the remaining length of the wire, where
 $L_2 = 100 - L_1$

NOTE ↓

* Balance Condition in the Metric Bridge:

→ At the balance point, the voltage difference across the galvanometer is zero, so:

$$R_x \times L_2 = R \times L_1$$



Very important↓

Objective of the Experiment:

1. To determine the unknown resistance
2. Determination of the specific resistance
3. Study the series and parallel connection

R (Ω)	1	2	3	4	5
L1 (cm)	21.0	27.0	28.5	30.0	31.0
$L2 = (100 - L1) \text{ (cm)}$	79.0	73.0	71.5	70.0	69.0
L1/L2	0.266	0.37	0.399	0.429	0.449
$R_x = (R \times L1/L2) \text{ (Ω)}$	0.266	0.74	1.197	1.716	2.245

مقاومة الخواص R_x و L_1 في دوائر القياس

